

Figure 1: Node 1 PCB design. This design does not include CAN interrupts and status LED.

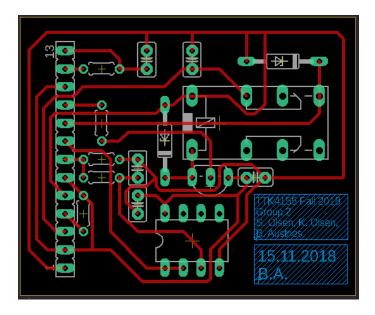


Figure 2: IR and solenoid control PCB design. Final version.